

RTL CHALLENGE

DAY-3 : Verilog Code for Implementation of 3 Inputs of Basic Logic Gates in GateLevel and DataFlow.

Software used : Xilinx Vivado(2023.1)

BASIC GATES :

AND GATE, OR GATE, NOT GATE, NAND GATE, NOR GATE, XOR GATE, XNOR GATE

By using these gates to implement the RTL schematic and waveform in Xilinx Vivado (2023.1) software

DATA FLOW :

DESIGN CODE:

```
// Design Name:
// Module Name: basicthreeinputgates

module basicthreeinputgates(
    input a,b,c,
    output andout,orout,norout,nandout,xorout,xnorout
);

    assign andout = (a&b&c);
    assign orout = (a|b|c);
    assign norout = !(a|b|c);
    assign nandout = !(a&b&c);
    assign xorout = (a^b^c);
    assign xnorout = !(a^b^c);

endmodule
```

TEST BENCH :

```
} // Design Name: Gate Level
} // Module Name: basicgatesusinggatelevel_tb

} module basicgatesusinggatelevel_tb();
  reg a;
  reg b;
  wire andout,orout,notout,xorout,nandout,norout,xnorout;
  basicgatesusinggatelevel uut (.a(a),.b(b),.andout(andout),.orout(orout),.
  notout(notout),.xorout(xorout),.nandout(nandout),.norout(norout),.xnorout(xnorout));


} initial
}   begin

    a=0;b=0;#100;
    a=0;b=1;#100;
    a=1;b=0;#100;
    a=1;b=1;#100;


}   end

} endmodule
```

RTL SCHEMATIC :

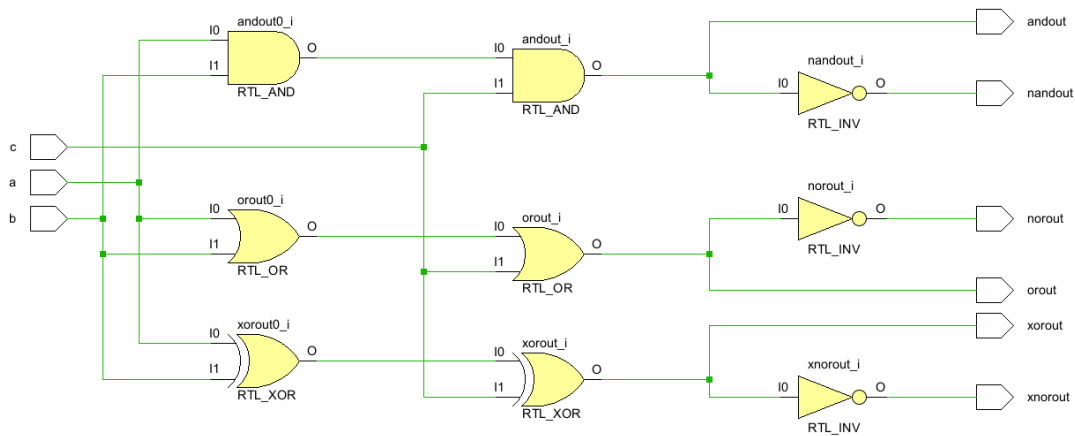

WAVE FORM:-

 

GATE LEVEL :

DESIGN CODE:-

```
//Gate Level
module basicthreeinputgate1(
    input a,b,c,
    output andout,orout,norout,nandout,xorout,xnorout
);

    and(andout,a,b,c);
    or(orout,a,b,c);
    nor(norout,a,b,c);
    nand(nandout,a,b,c);
    xor(xorout,a,b,c);
    xnor(xnorout,a,b,c);


endmodule
```

TEST BENCH :-

```
module basicthreeinputgate1_tb();
    reg a,b,c;
    wire andout,orout,norout,nandout,xorout,xnorout;
    basicthreeinputgate1 uut (andout,orout,norout,nandout,xorout,xnorout,a,b,c);

    initial
        begin
            a=0;b=0;c=0;#100;
            a=0;b=0;c=1;#100;
            a=0;b=1;c=0;#100;
            a=0;b=1;c=1;#100;
            a=1;b=0;c=0;#100;
            a=1;b=0;c=1;#100;
            a=1;b=1;c=0;#100;
            a=1;b=1;c=1;#100;
        end
endmodule
```

RTL SCHEMATIC :-

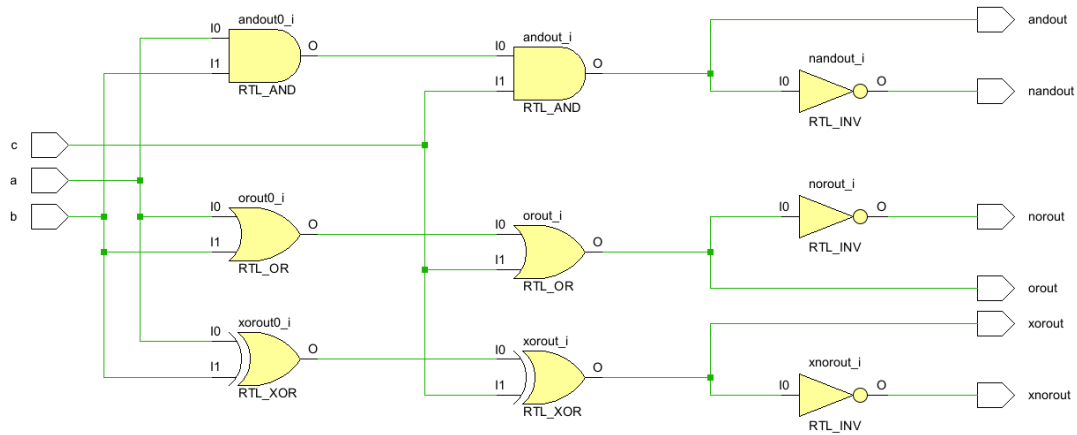

WAVE FORM :

